

Student 1 – name

Student 2 – name

Group

Date/Time

Table nbr.

Worksheet 4 - Lab 41. a) $R =$ $C =$ $f_{-3dB\ calc} =$ b) $f_{-3dB} =$

c)

$U_{i\text{dB}}$	-5dB	0dB	5dB
$U_{o\text{dB}}$			

Explanation:

2. a)

LPF	$f_{-3dB}/10$	$f_{-3dB}/4$	$f_{-3dB}/2$	f_{-3dB}	$2f_{-3dB}$	$4f_{-3dB}$	$10f_{-3dB}$
Frequency [kHz]							
$U_{i\text{dB}}$							
$U_{o\text{dB}}$							
$ H(\omega) _{dB}$							

b) in the *stopband*, roll-off [dB/decade]=

roll-off [dB/octave]=

Explanation:

3. a) $f_{-3dB} =$

4. a)

HPF	$f_{-3dB}/10$	$f_{-3dB}/4$	$f_{-3dB}/2$	f_{-3dB}	$2f_{-3dB}$	$4f_{-3dB}$	$10f_{-3dB}$
Frequency [kHz]							
$U_{i\text{dB}}$							
$U_{o\text{dB}}$							
$ H(\omega) _{dB}$							


b) in the *stopband*, roll-off [dB/decade]=

roll-off [dB/octave]=


Explanation:

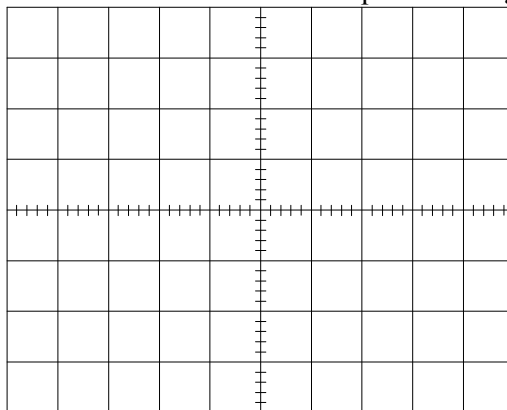5. . $\tau = RC =$ $T_1 =$ $T_2 =$ $T_3 =$ $f_1 =$ $f_2 =$ $f_3 =$

OBS: draw the arrows which correspond to the ground level



Response of integrator circuit (3 cases)

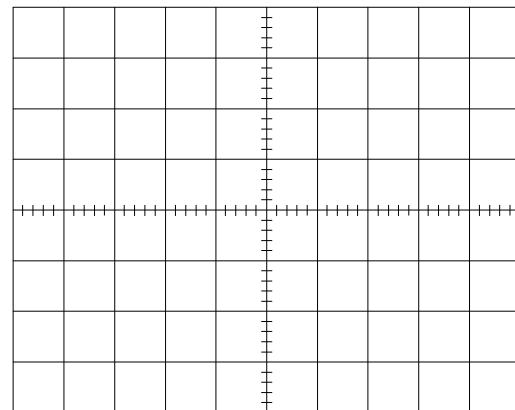

Response of differentiator circuit (3 cases)

5. Explanations:

2c, 4c: Amplitude-frequency plots for the LPF and HPF

In order to represent a log-frequency scale you could take into account that: $\lg 2 \approx 0,3$; $\lg 3 \approx 0,48$; $\lg 4 \approx 0,6$; $\lg 5 \approx 0,7$; $\lg 6 \approx 0,78$; $\lg 7 \approx 0,84$; $\lg 8 \approx 0,9$; $\lg 9 \approx 0,95$.

